

CSE 2600

Intro. To Digital Logic & Computer Design

Bill Siever
&
Michael Hall

Reminder


- Studios can (and should) be done collaboratively!
- Homework should be done *independently*
 - Ok to discuss *ideas* and related work from *studio*
 - Should not discuss / share details of specific solutions


This week & misc.

- Hw1 returned: Regrade requests open for 1 week
- Hw #3B Posted / Due Sunday
 - Can re-submit autograder stuff
- Exam 1: Next Thursday during class
 - Exam 1 page: <https://washu-cse2600-sp26.github.io/events/exam1>
- Next Tuesday: Exam Review
 - TAs likely to have exam review ~7pm on Feb. 18th too (McDonnell 361?)

Last Lecture

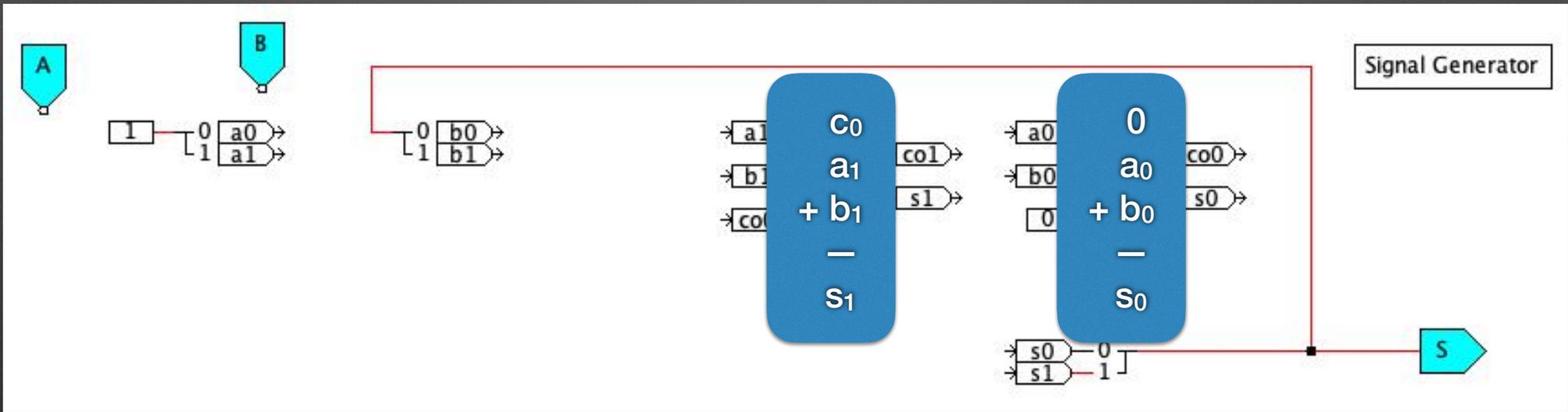- Sequential Circuits: Have a loop and outputs impact the inputs
 - Loopy adder



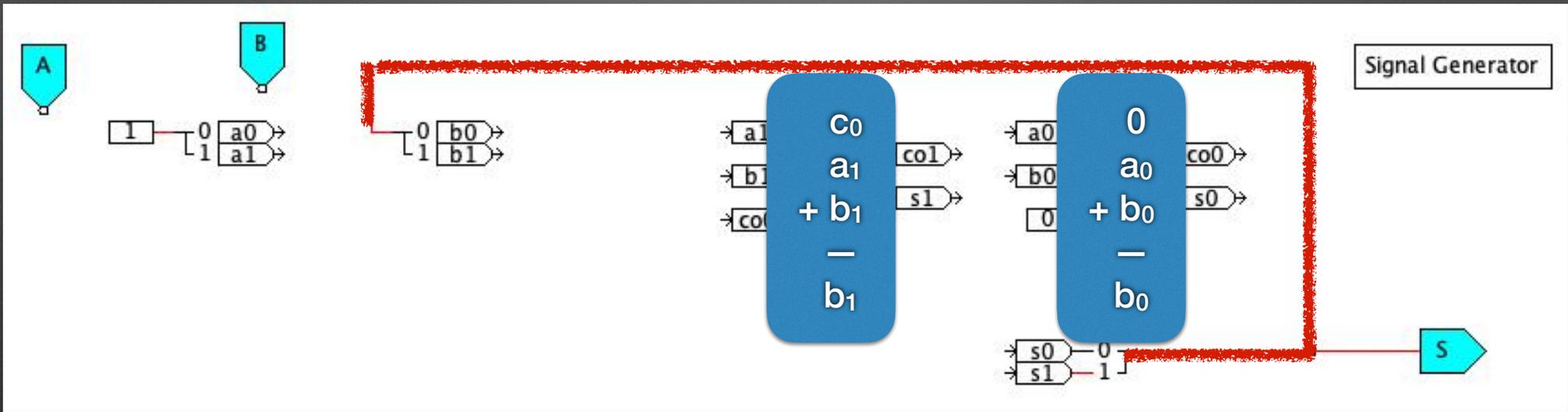

Last Lecture

- Bistable: Will hold one of two different states
 - May have some “metastable” condition (oscillating or between 1/0)
- SR-Latch: Cross-coupled NOR version
 - JLS version & time
 - Racing and unpredictable behavior

SR Latch Issues: Hazardous Conditions!

- Short pulse
- R & S dropping at the same time


Last Lecture

- D Latch: Transparent on high clock
- D Flip-Flop: Two D-latches that are transparent at opposite clock levels
 - Provide precise timing of data *acquisition* / storage
 - General focus: positive/rising edge triggers

D Flip Flop can be built from SR Latches


- Internal latch
 - Fails if pulses too short
 - Unstable if R/S drop at same time / too close
- Setup Time: Time needed before clock to ensure stable capture
- Hold Time: Time After clock edge value must be “held”

D-Flip-Flop Clock

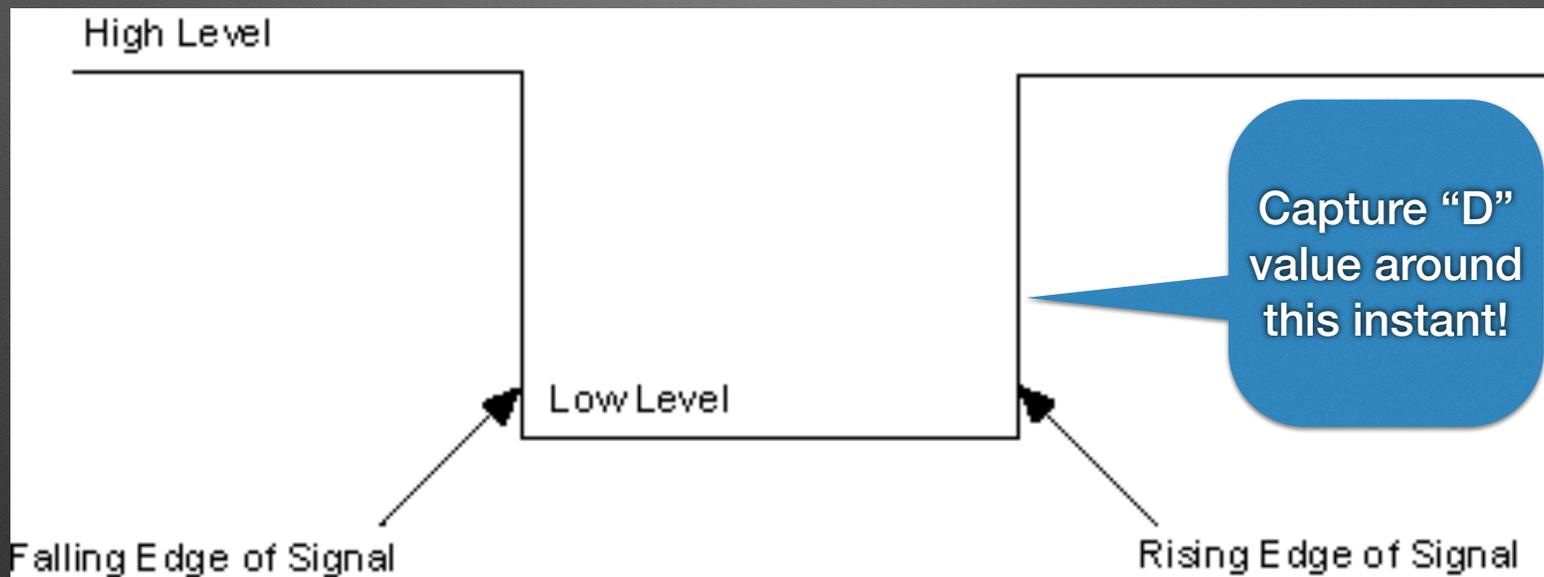

https://www.ni.com/docs/en-US/bundle/ni-hsdio/page/hsdio/fedge_trigger.html

Dff: Setup & Hold Time

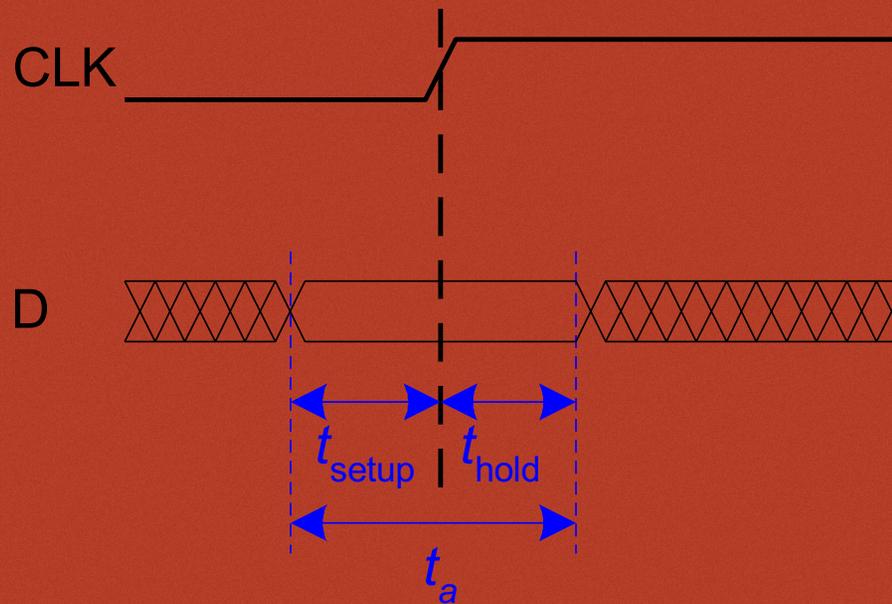


D Flip Flop Time Parameters


- t_{setup} : Time D must be stable before clock
- t_{hold} : Time D must be stable after clock
- t_a : Aperture time ($t_{setup} + t_{hold}$) —
total window of time D needs to be stable around clock

Dff Time Parameters Relative to Clock

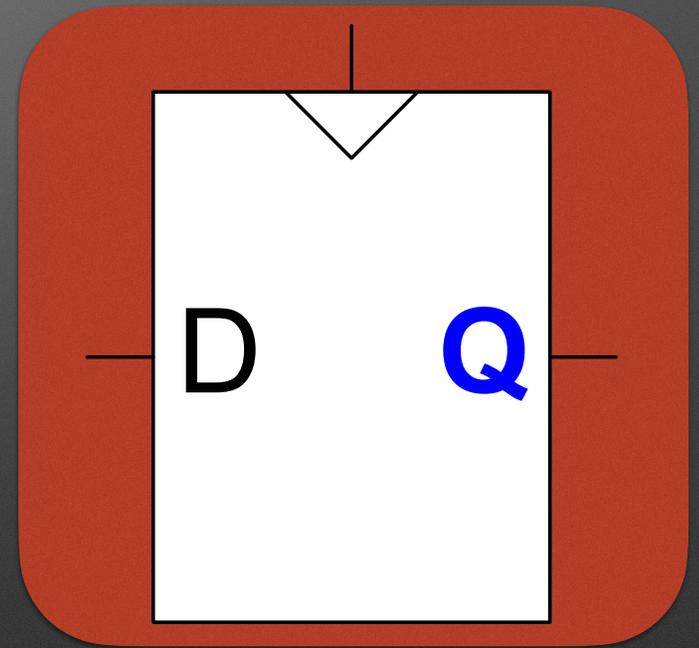- t_{pcq} : Propagation delay from Clock to Q (pcq)
- t_{ccq} : Contamination delay from C to Q (ccq)



Flip-Flop Timing Parameters

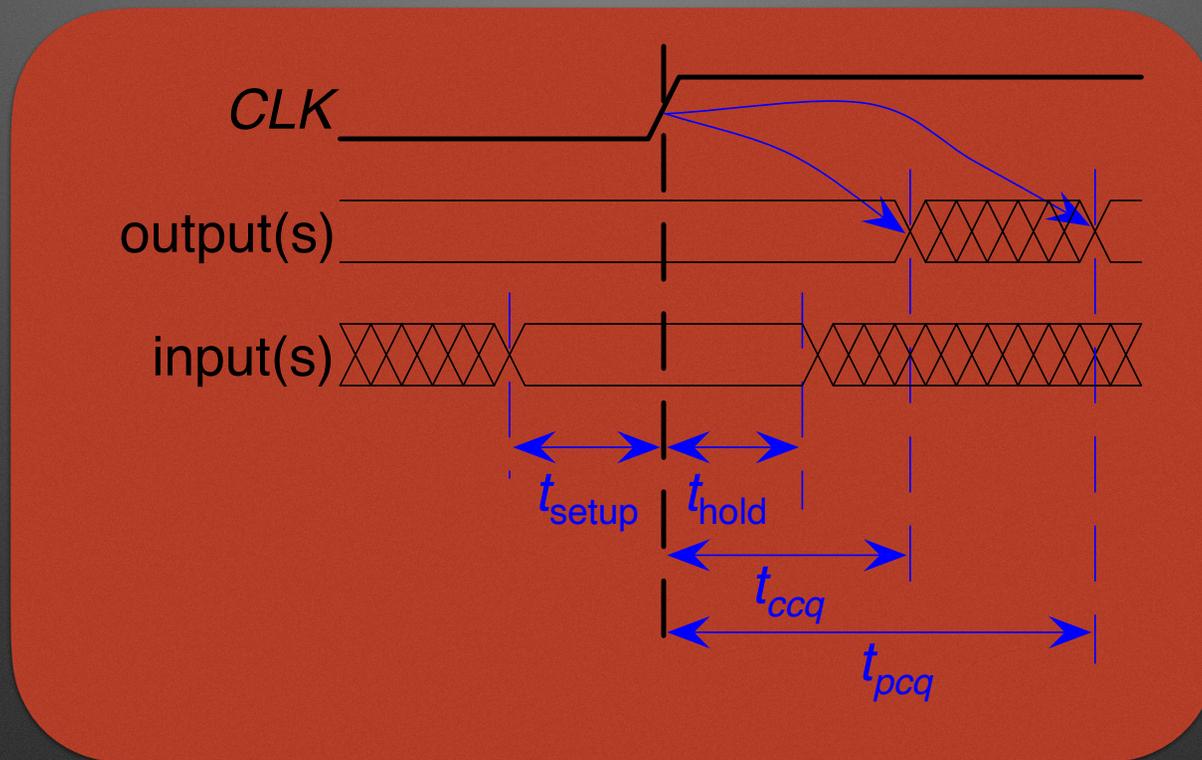


Sequential & Synchronous Logic


- Sequential circuits
 - Can't be represented with a *simple* table of just inputs and outputs (Possibly a complex table of history of inputs and outputs)
 - Output depends on sequence of inputs and timing
- Synchronous Sequential Circuits
 - Sequential circuits with additional restrictions on form to improve predictability

Synchronous Sequential Circuits

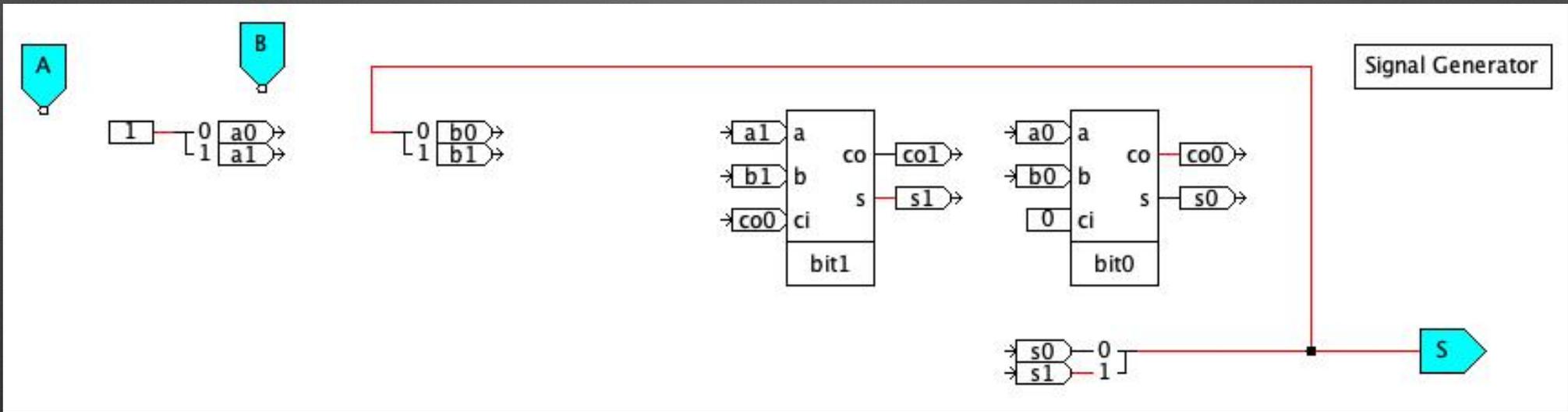- Are *synchronized* by a common clock
- Uses registers (*D Flip-Flops*)
- Mix of registers and combinational logic
- All cycles in circuit include *at least one register*
- Goal: Impose predictable behavior!




Loopy Adder w/ Synchronous

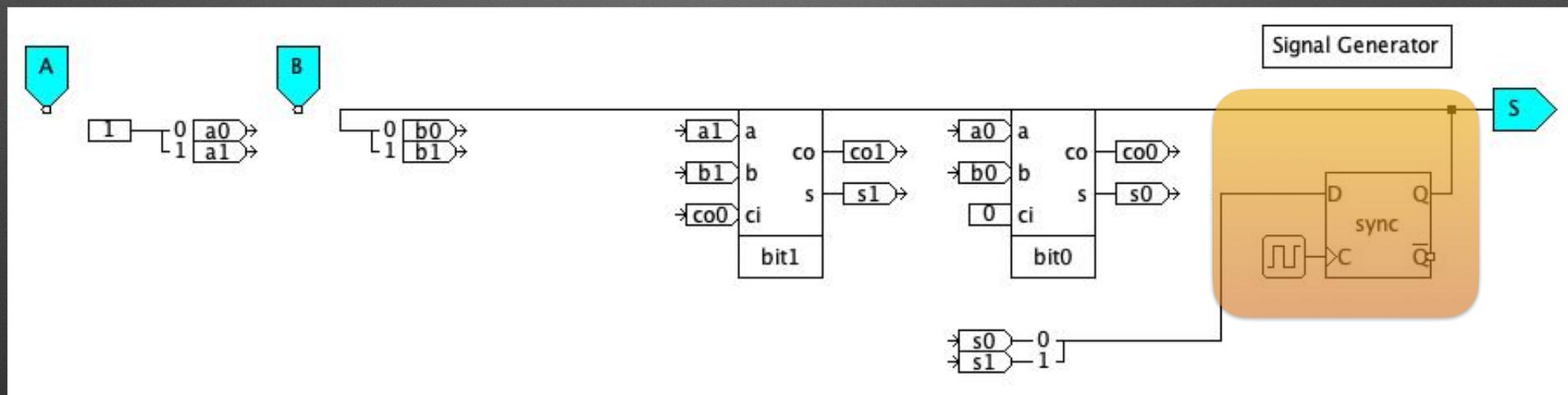


Finite State Machines

- Can be realized with *synchronous* sequential circuits
 - Memory (registers/flip-flops) hold *encoded* state (represents the location or current bubble in diagram)
 - Combinational logic for:
 - Output control (the outputs in the bubbles)
 - Determine next state (the arrows)

FSM: Moore Machine Structure

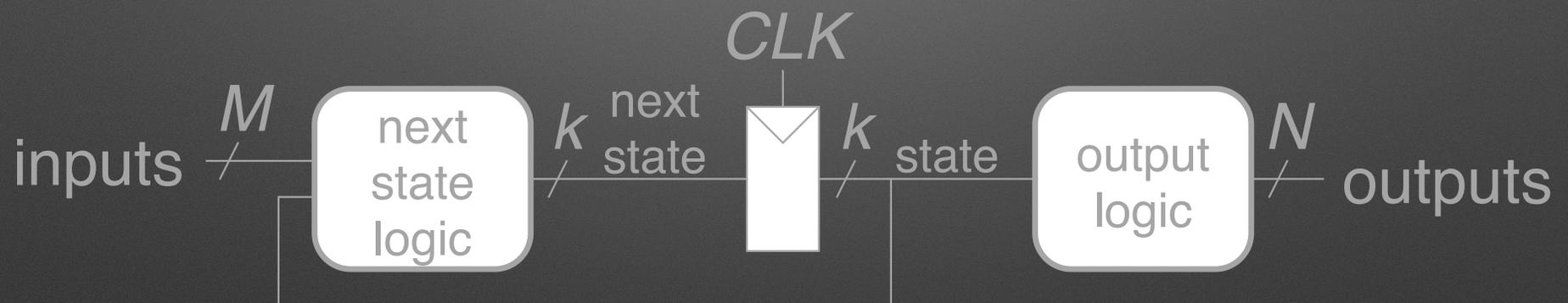

FSM: Mealy Machine

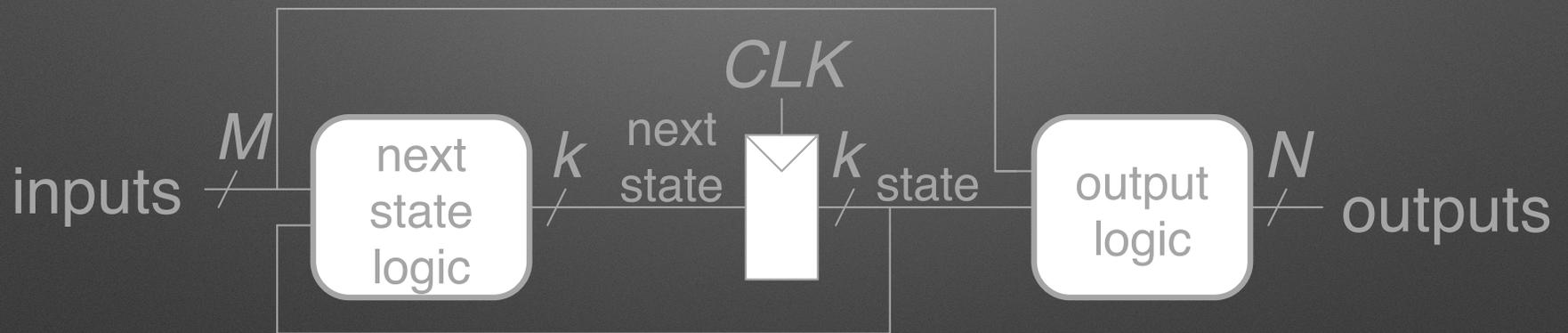


FSM Applications

- Things with modes or sequences of steps. Examples:
 - Washing Machine (fill, agitate, rinse, spin)
 - Stop lights & Traffic control: Green, Yellow, Red
 - Locks: Locked & unlocked
 - Computer programs: Playing game vs. on menu
 - Elevator controls (state = floor)
 - ...

Studio 3A Summary

- 74F175: Memory/storage, bits, and resets
- Elevator Example

Overall

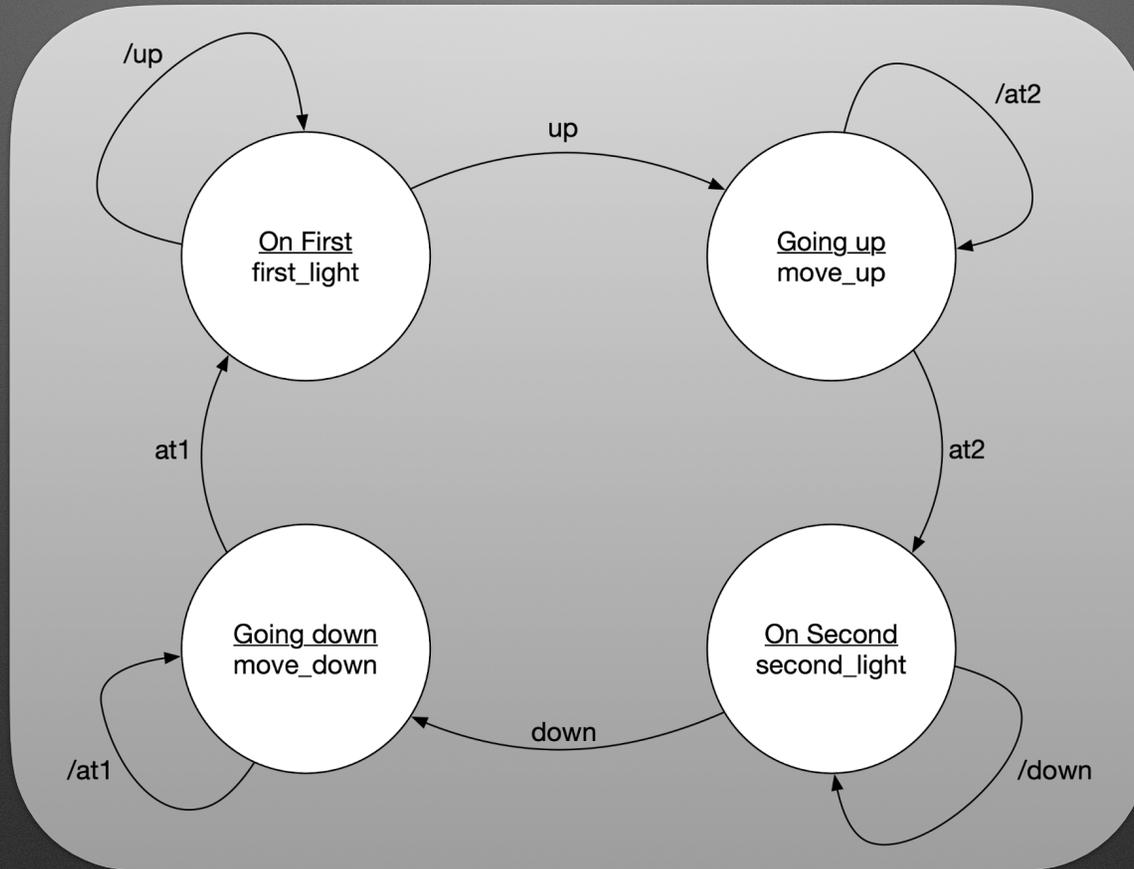

Overall State Encoding


State Name	Numeric Encoding	State Bits	
		S1	S0
On first	0	0	0
Going up	1	0	1
On second	2	1	0
Going	3	1	1

Output Decisions (based on state)


State Name	Numeric Encoding	State Bits		Outputs				
		S1	S0	move_up	move_down	first_light	second_light	moving
On first	0	0	0	0	0	1	0	0
Going up	1	0	1	1	0	0	0	1
On second	2	1	0	0	0	0	1	0
Going down	3	1	1	0	1	0	0	1

Output Equations

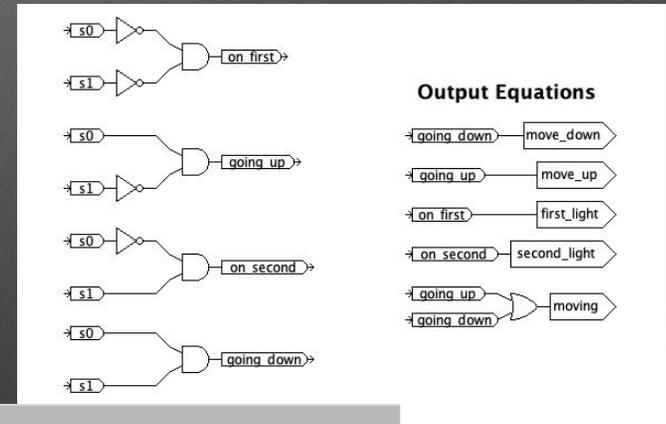
$$\begin{aligned} \text{move_up} &= \text{Going_up} = /S1 * S0 \\ \text{move_down} &= \text{Going_down} = S1 * S0 \\ \text{first_light} &= \text{On_First} = /S1 * /S0 \\ \text{second_light} &= \text{On_Second} = S1 * /S0 \\ \text{moving} &= \text{Going_up} + \text{Going_down} = /S1 * S0 + S1 * S0 \end{aligned}$$



Output Equations

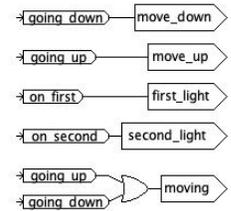

Overall

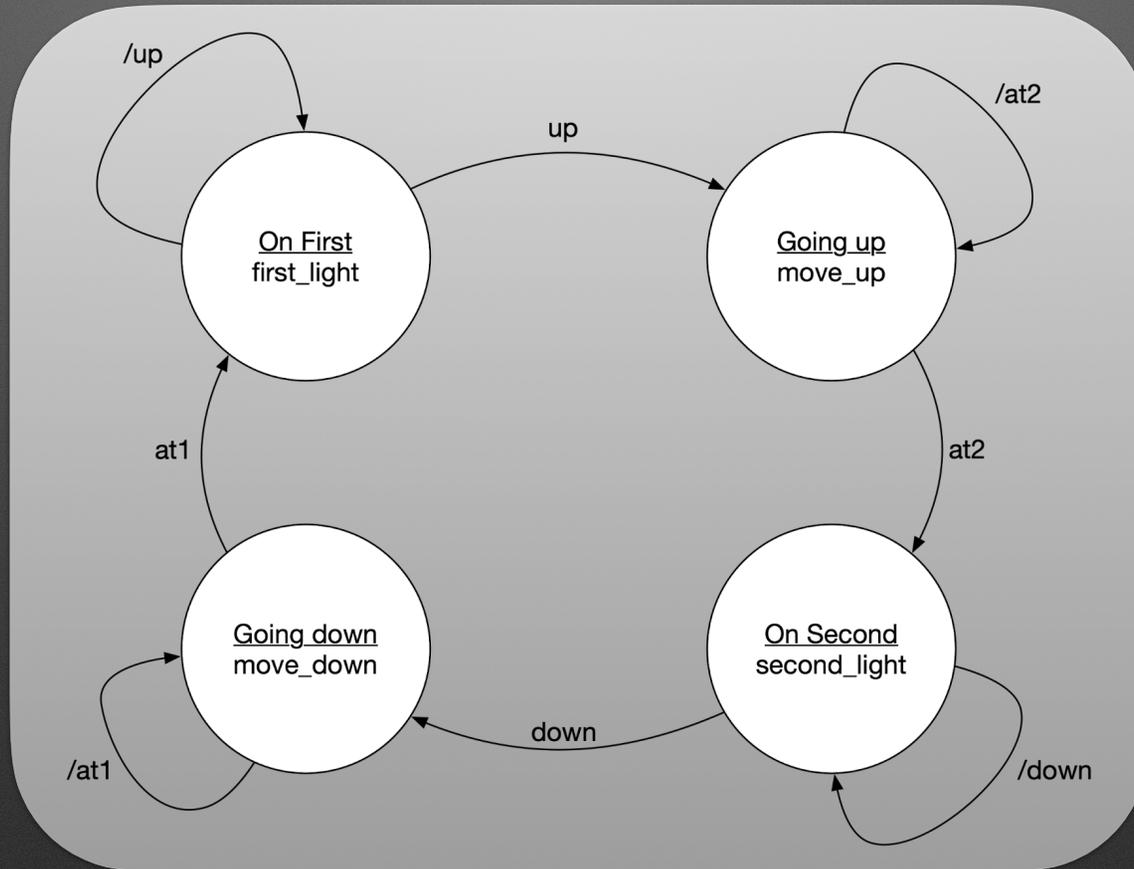


Overall

State Encoding

State Name	Numeric Encoding	State Bits	
		S1	S0
On first	0	0	0
Going up	1	0	1
On second	2	1	0
Going	3	1	1


Next State Equations
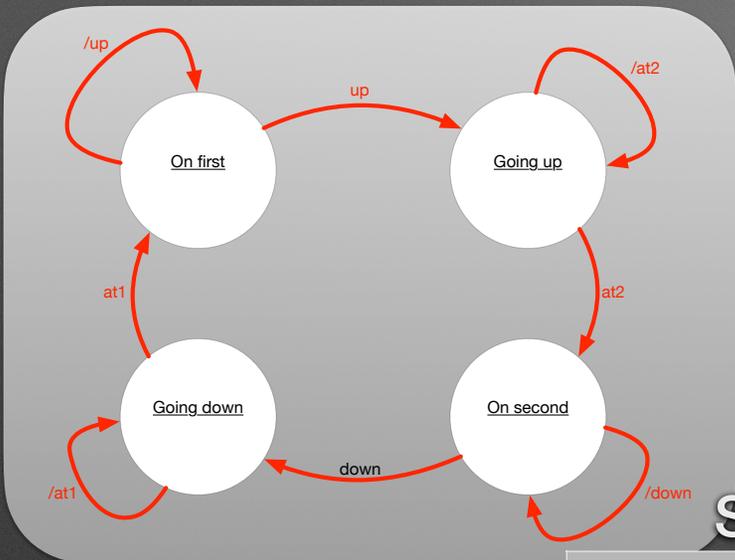
$$\begin{aligned}
 ns1 &= On_Second * at2 + \\
 &\quad On_second * /down + \\
 &\quad Going_down * down + \\
 &\quad Going_down * /at1 \\
 ns0 &= Going_up * up + \\
 &\quad Going_up * /at2 + \\
 &\quad On_second * down + \\
 &\quad Going_down * /at1
 \end{aligned}$$




State Transitions (to "next state")

State Name	Numeric Encoding	Inputs				Next State		
		up	down	at1	at2	Name	ns1	ns0
On first	0	0	X	X	X	On_first	0	0
		1	X	X	X	Going_up	0	1
Going up	1	X	X	X	0	Going_up	0	1
		X	X	X	1	On_second	1	0
On second	2	X	0	X	X	On_second	1	0
		X	1	X	X	Going_down	1	1
Going down	3	X	X	0	X	Going_down	1	1
		X	X	1	X	On_first	0	0

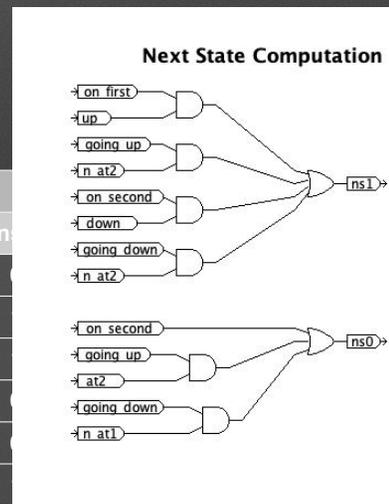


Overall Structure

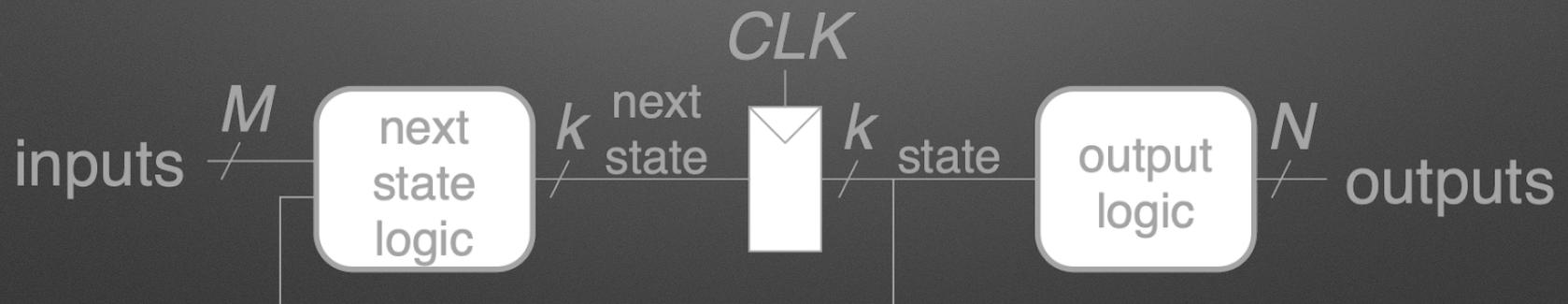


Overall Implementation


Inputs (to named wires)

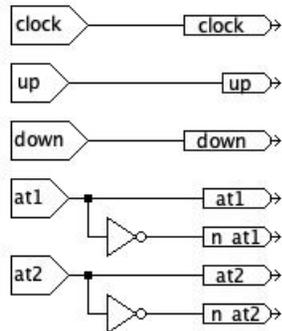


Next State Computation

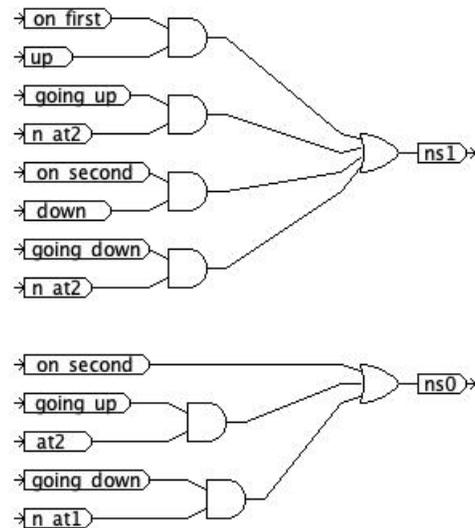


State Storage and Decoding

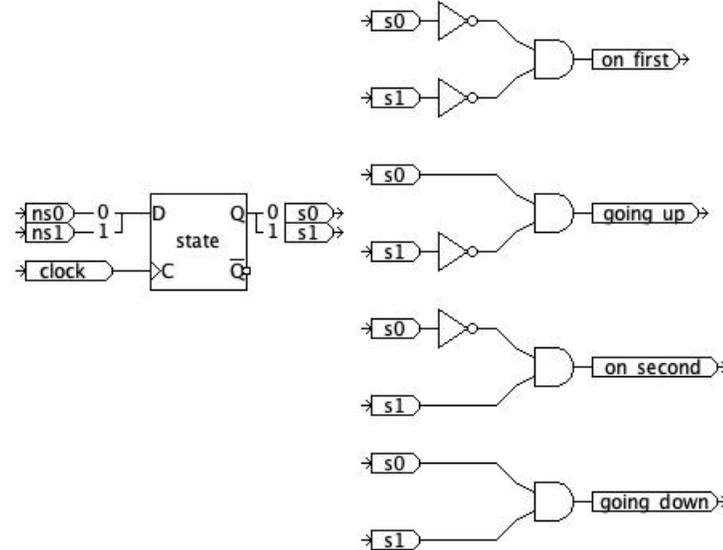

Output Equations

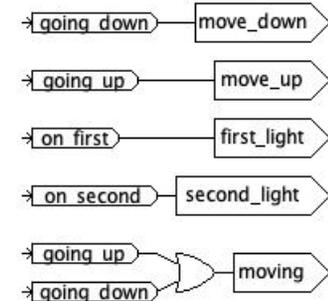


Overall Implementation

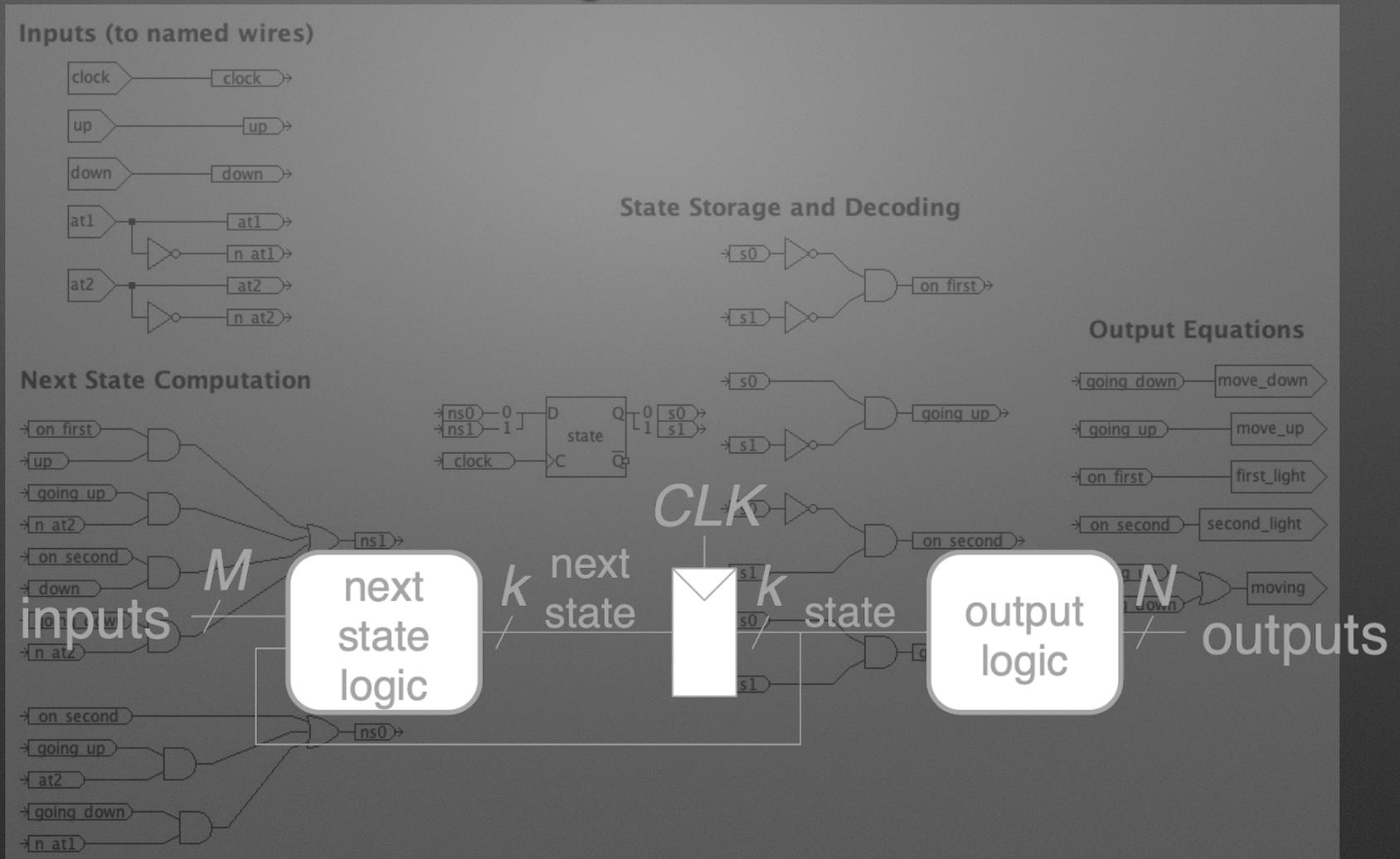


Overall Implementation

Inputs (to named wires)

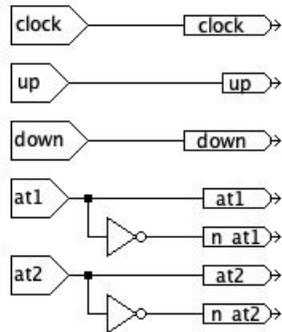

State Storage and Decoding

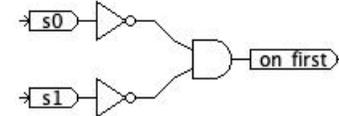

Output Decisions
(based on state)

Next State Computation




State Transitions (to "next state")

State Name	Numeric Encoding	Inputs				Next State		State Bits		Outputs		
		up	down	at1	at2	Name	ns1	ns0	move_up	move_down	first_light	second_light
On first	0	0	X	X	X	On_first	0	0	0	0	1	0
Going up	1	X	X	X	0	Going_up	0	1	0	1	0	0
On second	2	X	0	X	X	On_second	1	0	1	0	0	1
Going down	3	X	0	X	X	Going_down	1	1	1	1	0	0

State Machine Diagram: Studio

Assume
clock cycle of
10s?

What does
"clock" do?

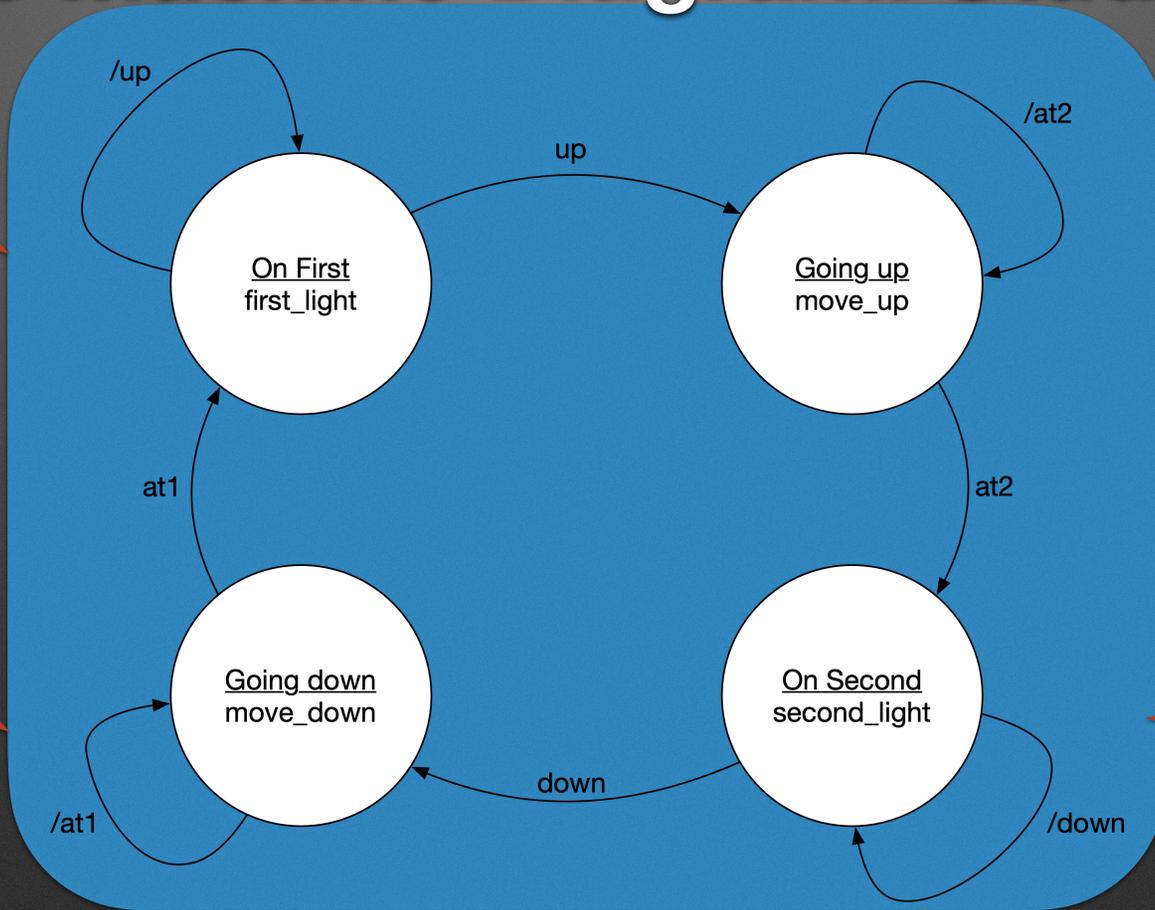

Vs 240s?

Can the
clock be too
short?

State Encodings

- “Art”
 - Encoding has impact on equations used
- Major flavors
 - Counting
 - One Hot

Elevator: Examples

STATE NAME	BINARY COUNTING	ONE HOT
ON FIRST		
GOING UP		
ON SECOND		
GOING DOWN		



Elevator: Examples Part 2

STATE NAME	BINARY COUNTING	ONE HOT
ON FIRST		
GOING UP		
ON SECOND		
GOING DOWN		


Decoder

- Decoders...decode
 - n bits of input to 2^n distinct, mutually exclusive outputs
 - It's just ANDs/NOTs to select each distinct binary value


Storage and Decoding

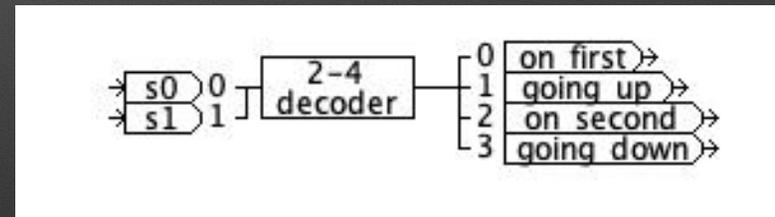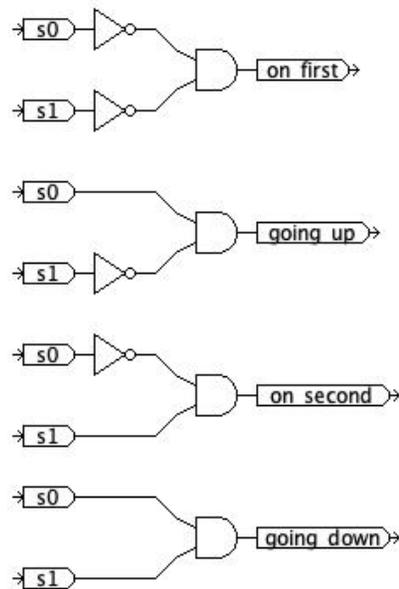


Review: Moore Machine Structure

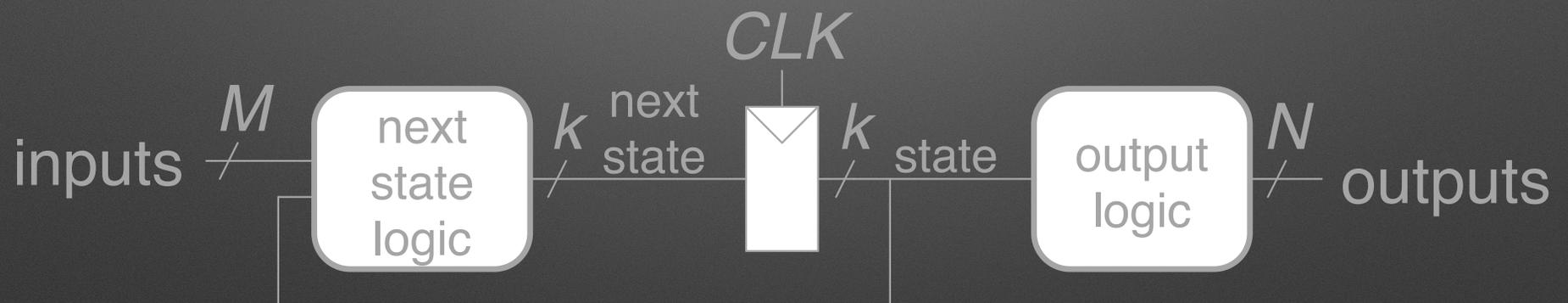

Review: Moore Machine Structure

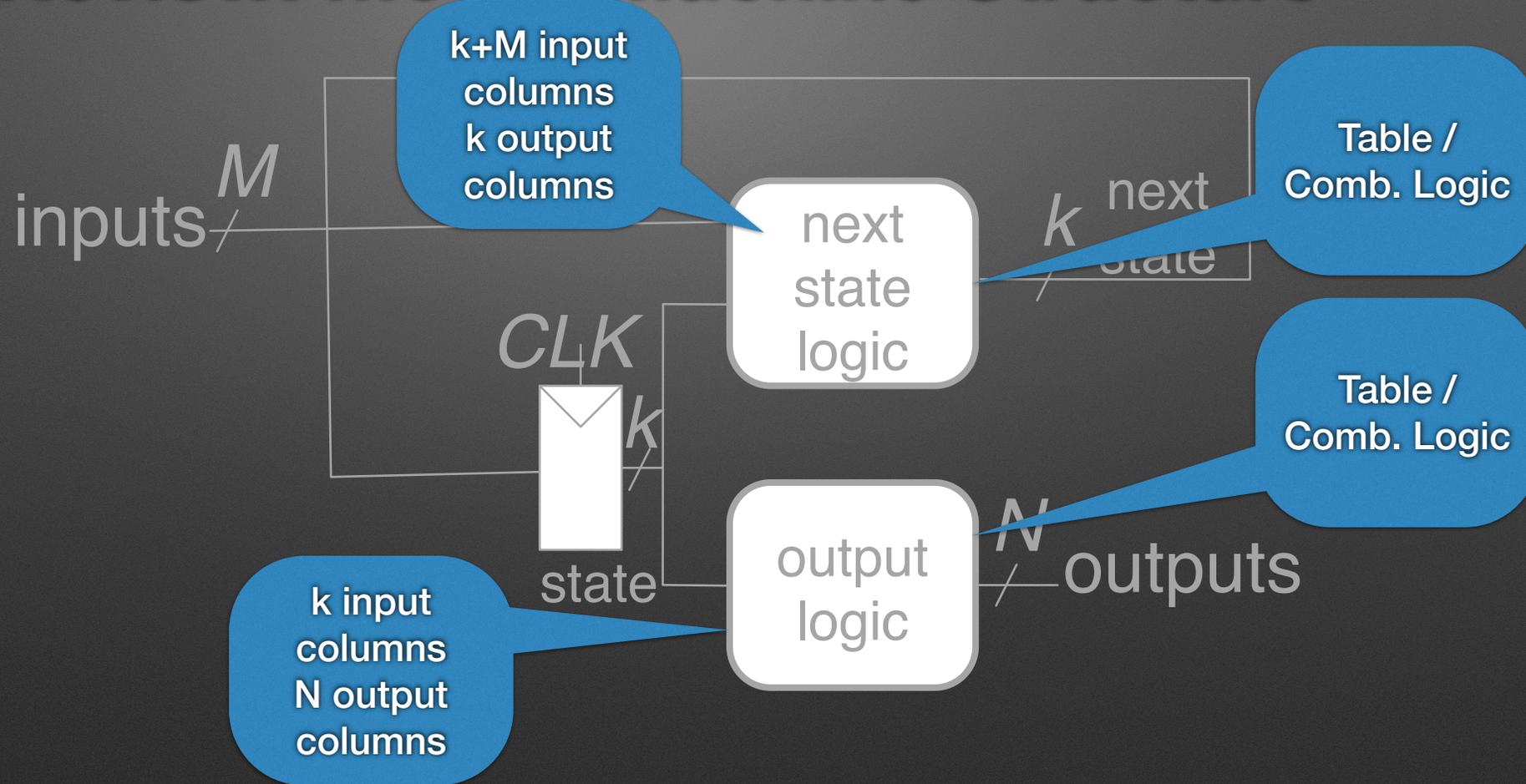



Review: Dff Setup & Hold Time

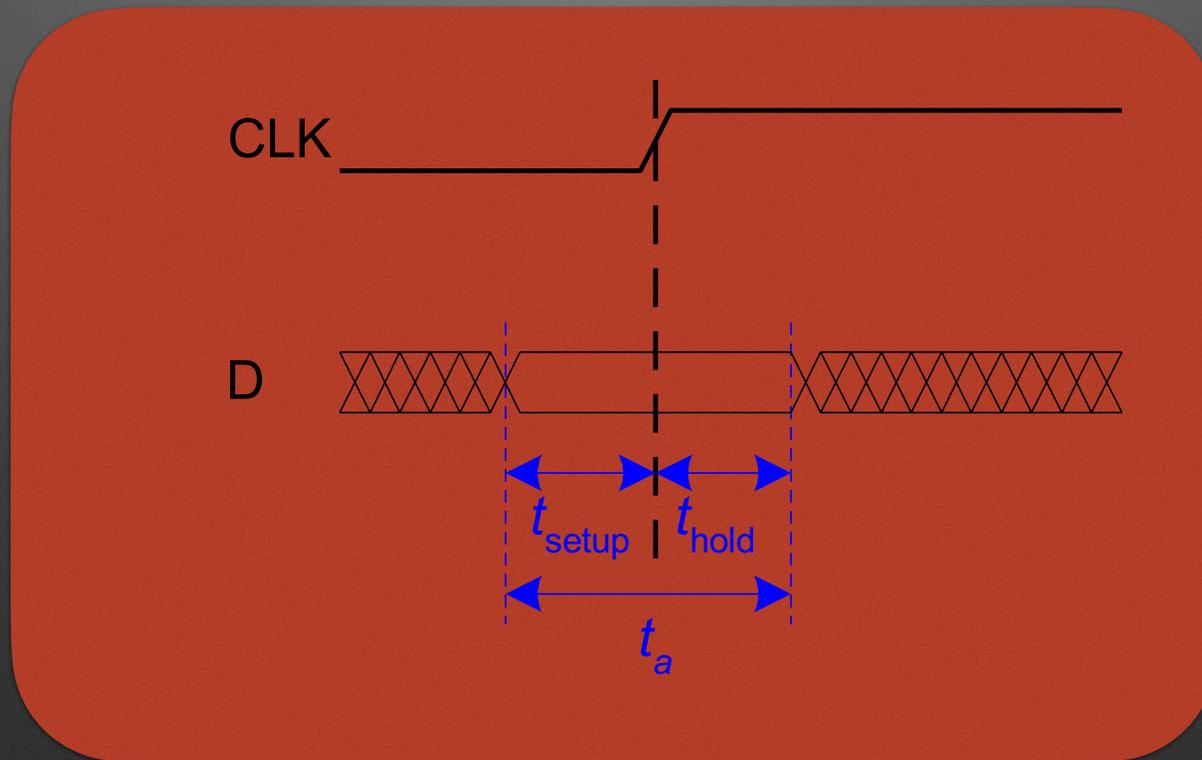

Dff Time Parameters

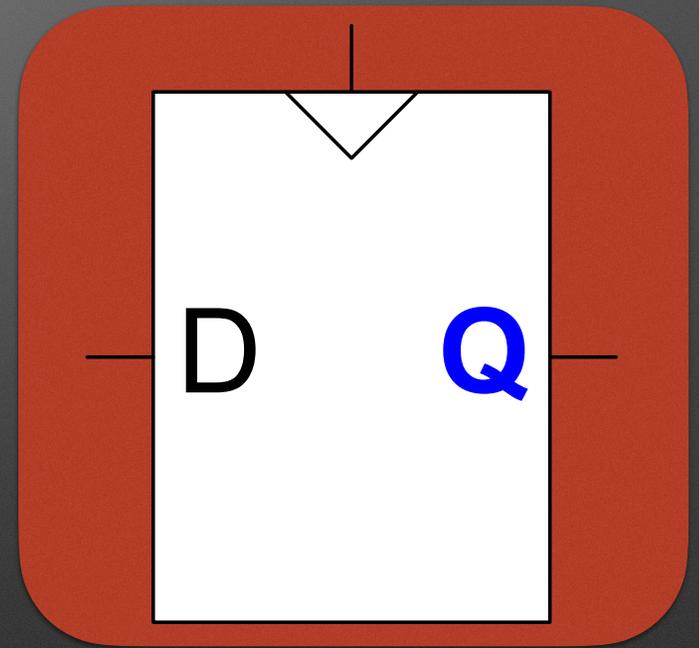
- t_{pcq} : Propagation delay from Clock to Q (pcq)
- t_{ccq} : Contamination delay from C to Q (ccq)



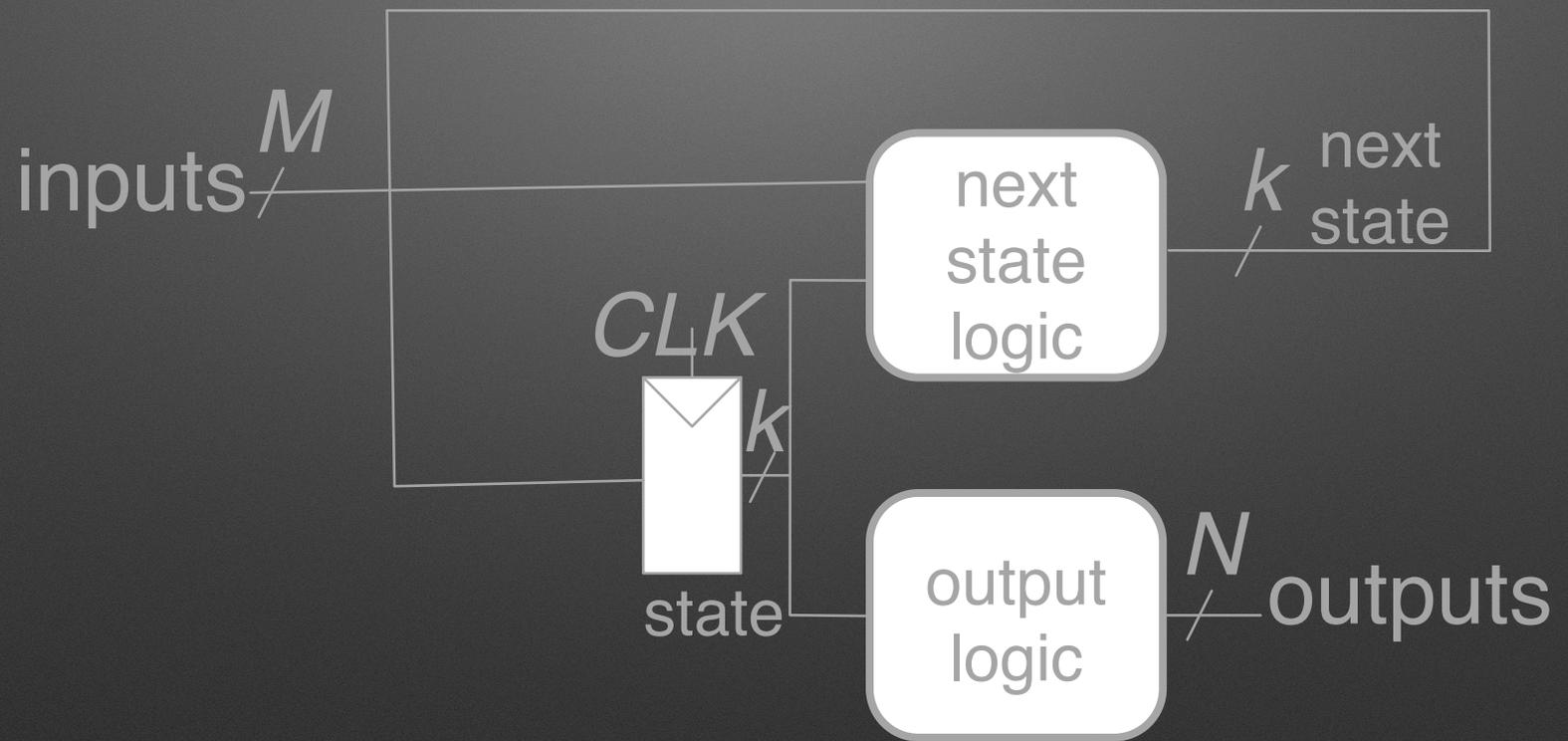


Setup Time Constraint

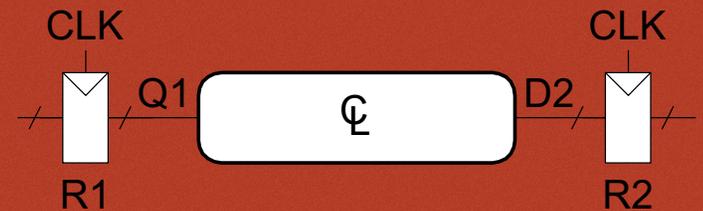- Max time from R1 through CL
- R2's input needs to be stable t_{setup} before clock




Setup Time Constraint

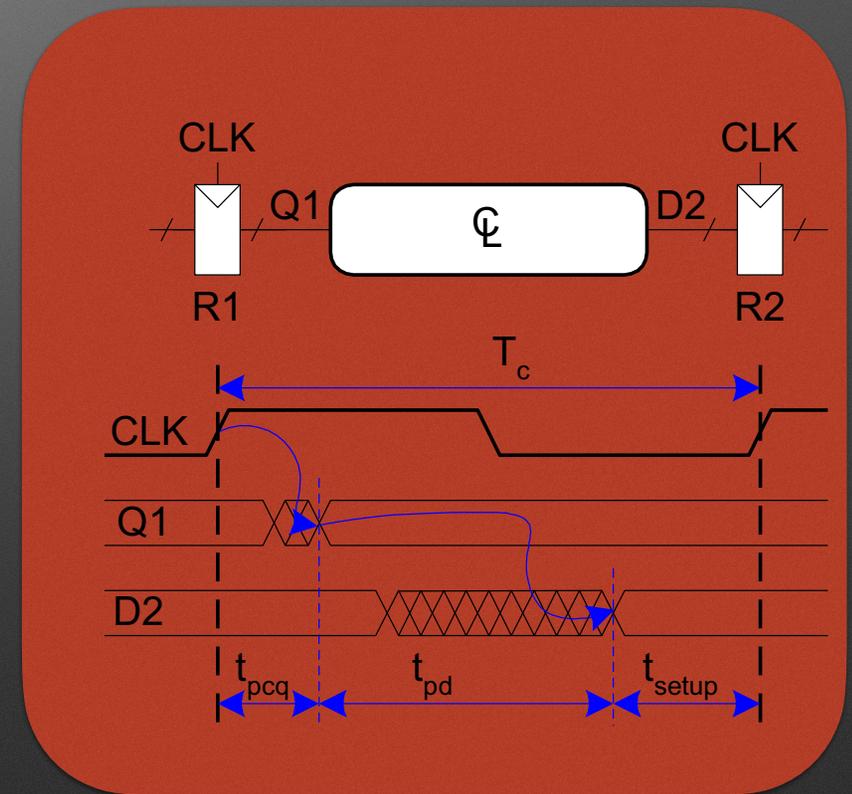- Max time from R1 through CL
- R2's input needs to be stable t_{setup} before clock




Hold Time Constraint

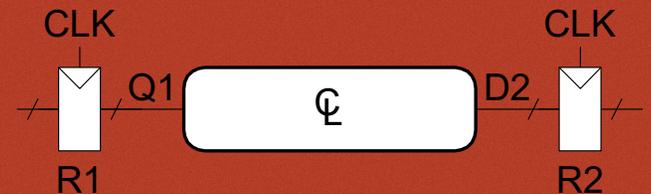- Min time from R1 through CL
- R2's input must be stable t_{hold} after the clock



Hold Time Constraint

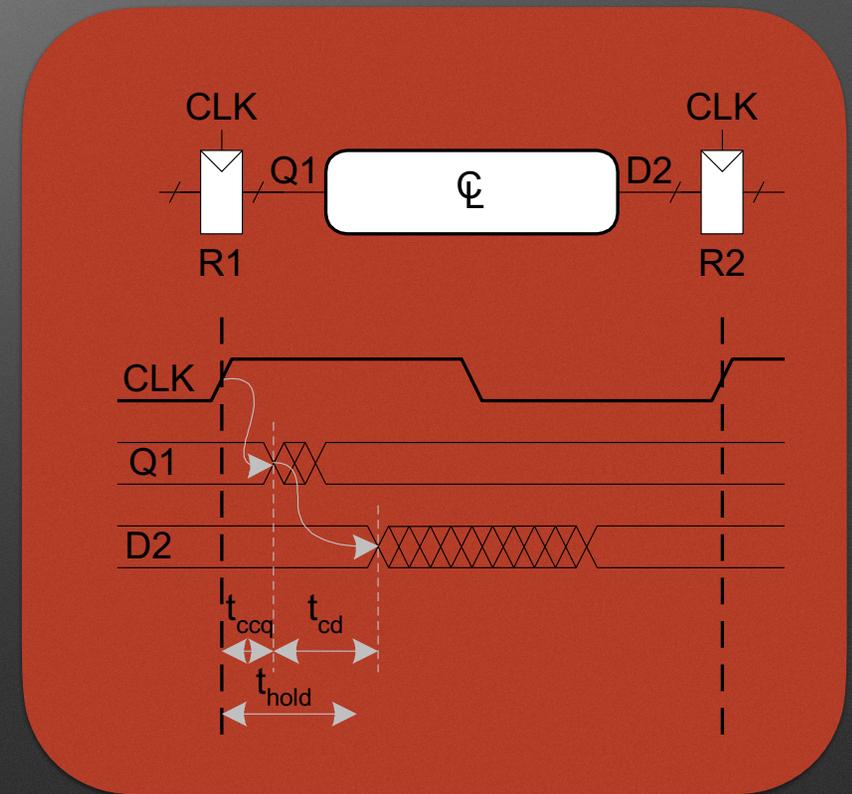- Min time from R1 through CL
- R2's input must be stable t_{hold} after the clock



Review: Moore Machine Structure



Too fast and t_{hold} violated!

Can slow it down with more logic/buffers

Too slow and t_{setup} violated!

Can slow down clock to accommodate t_{setup}

Synchronous Timing

- Must meet both
 - Setup Time Constraint
 - Hold Time Constraint

Next Time

- Studio